


$$\textcircled{1} \quad R = \frac{U}{I} \rightarrow I = \frac{U}{R} \rightarrow U = I \times R$$

a)

$$\textcircled{2} \quad V_i = 10V \quad R = 5k\Omega \quad 2R = 10k\Omega$$

$$R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$2R // 2R \rightarrow R_{eq} = \frac{2R \times 2R}{2R + 2R} = \frac{4R^2}{4R} = R$$

:

$$2R // 2R \Rightarrow R_{eq} = R$$

$$R = \frac{U}{I} \Leftrightarrow I = \frac{U}{R} \Leftrightarrow I = \frac{10}{5000} \Leftrightarrow I = 0,002A$$

$$P = U \times I \Leftrightarrow P = 0,002 \times 10 (= 1) P = 20mW$$

a)

$$\textcircled{3} \quad P = 35W \\ U = 12V$$

$$P = U \times I \Leftrightarrow 35 = 12 \times I \Leftrightarrow I = \frac{35}{12} \Leftrightarrow I = 2,92A$$

$$R = \frac{U}{I} \Leftrightarrow R = \frac{12}{2,92} \Leftrightarrow R = 4,11 \Omega \textcircled{1}$$

$$\textcircled{4} \quad I(11A) = -\frac{9}{9+2} \times 11 = -9A \textcircled{2}$$

$$\textcircled{5} \quad \frac{10}{3} = 3,3A \quad 33 - 0,67 = 2,66A \\ \frac{4}{6} = 0,67A \quad \frac{4}{2,66} = 1,5 \approx 2$$

$$\textcircled{6} \quad \frac{10mA}{0,5\mu F} = 20V \quad 20 \times 0,1 = 2V \textcircled{2}$$

\textcircled{7} b

$$\textcircled{8} \quad d \quad 4V \quad I_{R_1} = \frac{1}{2} I_{R_{23}} \quad 1\Omega = \frac{1V}{1A}$$

$$I_w = \frac{1V}{2\Omega} \Leftrightarrow I_{R_2} = 0,5A \quad 1 + 0,5 = 1,5A$$

$$4\Omega = \frac{4V}{1A} \Leftrightarrow V = 4V$$

$$\textcircled{9} \quad R_1 + R_2 = 16 \text{ k}\Omega$$

$$\frac{16 \times 4}{20} = \frac{64}{20} = \frac{32}{10} = 3,2 \text{ k} \quad \textcircled{c}$$

$$\textcircled{11} \quad Z_C = \frac{1}{j\omega C} \Leftrightarrow 2 \text{ k} = \frac{1}{j\omega \times 1 \times 10^{-6}}$$

$$\Leftrightarrow 2 \times 10^3 \times 10^{-6} = \frac{1}{j\omega}$$

$$\Leftrightarrow 2 \times 10^{-3} \omega = \frac{1}{j}$$

$$\Leftrightarrow 2 \times 10^{-3} \times \frac{2\pi}{T} = \frac{1}{j}$$

$$\Leftrightarrow \frac{4 \times 10^{-3} \pi}{T} = \frac{1}{j} \quad \text{et} \quad \frac{1}{250} \times \frac{\pi}{T} = \frac{1}{j}$$

$$\Leftrightarrow \frac{\pi}{250} \times j = \frac{1}{j} \quad \Leftrightarrow j = \frac{250 \times 1}{\pi} \quad \text{et} \quad j = 79,6 \text{ Hz}$$

$$\textcircled{5} \quad VR_1 = V_1 - V_2 = 10 - 4 = 6V$$

$$I_1 = \frac{VR_1}{R_1} = 2A$$

$$I_1 = I_2 + I_3 \Leftrightarrow I_3 = I_1 - I_2 \Leftrightarrow I_3 = 2 - \frac{4}{6}$$

$$I_2 = \frac{4}{6} A$$

$$\Leftrightarrow I_3 = \frac{12 - 4}{6} \Leftrightarrow I_3 = \frac{8}{6}$$

$$VR_3 = V_2 = R_3 I_3$$

$$U = R_3 \times \frac{8}{6} \Leftrightarrow R_3 = \frac{4}{\frac{8}{6}} \Leftrightarrow R_3 = \frac{4 \times 6}{8} \Leftrightarrow R_3 = \frac{24}{8} \Leftrightarrow R_3 = 3 \Omega$$

$$\textcircled{16} \quad 10 - 0,7 = 9,3 V$$

$$\frac{9,3}{10 \times 10^{-3}} \times 6 \times 10^3 = 5,58 V$$

$$\frac{5,58}{6 \times 10^3} = 0,93 \text{ mA} \quad \textcircled{c}$$

Teste 2018 - 19

① $P = V \times I$ (c)

② $R // 2R = \frac{R \times 2R}{R + 2R} = \frac{2R^2}{3R} = \frac{2R}{3}$ (5)

③ $I_1 = \frac{10k \times I}{(5k + 10k)}$ $I_2 = \frac{5k \times I}{(5k + 10k)}$

Fórmula: $\frac{R_1}{R_1 + R_2} \times I$ $I_1 = 2I_2$

④ Círculo - circuito da fonte de tensão:

$$V_A = (40//40) \times 2A \text{ (1)} \quad V_A = \frac{40 \times 40}{40+40} \times 2$$

$$\hookrightarrow V_A = 20 \times 2 = 40V$$

Abrimos a fonte: $V_B = \frac{10V \times 40\Omega}{40 + 40} = 5V$

$40 + s = 45V$ (B) de corrente

$$⑥ P = \frac{U^2}{R}$$

$$P = 10W$$

$$I_1 + I = I_2$$

$$10W = \frac{U^2}{R} \Leftrightarrow 10 \times 40 = U^2 \\ \Leftrightarrow 400 = U^2 \\ \Leftrightarrow U = 20V$$

$$I_2 = \frac{2\phi}{4\phi} \Leftrightarrow I_2 = 0,5A$$

$$I_1 + I = 0,5A \quad \leftarrow I = 0,5A + 0,25A \Leftrightarrow I = 0,75A$$

$$I_1 = \frac{10 - 20}{40} \Leftrightarrow I_1 = -0,25A$$

$$I_1 = \frac{10 - V_2}{R_1}$$

$$⑤ P = \frac{U^2}{R} \Leftrightarrow 2\Omega$$

$$I = \frac{U}{R}$$

$$I_1 + 6A = I_2$$

$$V_1 = 0,5V_0 - V_0 = -0,5V_0$$

$$\frac{V_1}{1\Omega} + 6A = \frac{V_0}{2\Omega} \Leftrightarrow -0,5V_0 + 6A = \frac{V_0}{2} \Leftrightarrow -V_0 + 12 = V_0 \Leftrightarrow V_0 = 6V$$

$$\downarrow \\ \frac{V_1}{I_1} = I_2$$

$$P = \frac{36}{2} = 18W \quad \textcircled{E}$$

$$\textcircled{7} \quad V_{(ac)} = \frac{2k}{(V_1 + V_2 \text{ ou } V_1/V_2)} \times \begin{matrix} \text{Voltage em da fonte de} \\ \text{tensão} \end{matrix}$$

$$V_{th} = V(30k) = \frac{30k}{20k+30k} \times 10V = V(30k) = 6V$$

Certo circuitando a fonte:

$$R_{th} = 8k + (30k//20k) = 8k + \frac{30k \times 20k}{30k+20k}$$

$$= 8k + \frac{600k}{50} = 8k + 12k = 20k\Omega$$

$$V_{th} = 6V \text{ e } R_{th} = 20k\Omega$$

\textcircled{8} Certo circuitando a saída:
(quando a corrente é nula em 30kΩ)

$$I_m = \frac{10V}{20\Omega} = 0,5A = 500mA$$

Certo circuitando a fonte de tensão:

$$R_m = 30//20 = \frac{30 \times 20}{30+20} = 12\Omega$$



$$\textcircled{10} \quad f = \frac{1}{T} \Leftrightarrow f = \frac{1}{2\pi \times 10^{-3}} \Leftrightarrow f = 50 \text{ Hz}$$

Valor eficaz: $V_e = \frac{V_{\text{Máx}}}{\sqrt{2}}$ $\Leftrightarrow V_e = \frac{325}{\sqrt{2}}$
 $\Leftrightarrow V_e = 230 \text{ V}$

R:C $\rightarrow 50 \text{ Hz}; 230 \text{ V}$

\textcircled{11} Incremento 1V/ms

$$t(1V) = 1 \text{ ms} \quad q-1 = 8 \text{ ms} \quad R:b$$

$$t(9V) = 9 \text{ ms}$$

\textcircled{12} Passa alto pois o condensador está em série com o trajeto de V_{im} para V_{out}

$$f_c = \frac{1}{2\pi RC} \Leftrightarrow f_c = \frac{1}{2\pi \times 2k \times 1 \times 10^{-9}} \Leftrightarrow f_c = 79577 \approx 80 \text{ kHz}$$

R:A

$$\textcircled{14} \quad C \quad V_0 = V_i \quad f_c \gg 2 \text{ kHz}$$

$$\textcircled{15} \quad \omega L = \frac{1}{\omega C} \rightarrow \omega^2 LC = 1 \rightarrow \omega^2 \times 10^{-4} \times 25 \times 10^{-9} = 1 \rightarrow \omega^2 = 632 \times 10^3$$

$$f = \frac{\omega}{2\pi} \Leftrightarrow f = \frac{632 \times 10^3}{2\pi} \Leftrightarrow f = 100 \text{ kHz}$$



$$13) V_2 = \frac{10V \times R_2}{R_1 + R_2} = 5V = V_2(0s) = V_{\text{inicial}}$$

$$V_2(1\text{ms}) = V_{\text{inicial}} \times e^{\frac{-T}{1\text{ms}}} = 5 \times e^{-1} = 1,84V$$

$$T = R_2 C \rightarrow T = 10^4 \times 10^{-9} = 10^{-5} = 1\text{ms}$$

só descarregamento por R_2

C

$$16) \underbrace{9,8 - 0,6 - 0,6}_{\begin{array}{l} \text{tensão} \\ \downarrow \\ \text{díodo} \end{array}} = \underbrace{(1k + R_2) \times 2\text{mA}}_{\text{Tensão em série}}$$

$$\approx 18,6 = (1k + R_2) \times 2\text{mA} \Leftrightarrow \frac{18,6}{2 \times 10^{-3}} = 1k + R_2$$

$$\Leftrightarrow 4300 = 1k + R_2$$

$$\Leftrightarrow R_2 = 3,3k \Omega$$

$$17) a) I = \frac{5}{2000} = 2,5\text{mA}$$

$$b) I = \frac{10}{4000} = 2,5\text{mA}$$

$$c) I = \frac{10}{3000} = 3,3\text{mA} \quad \leftarrow$$

$$d) I = 0A \text{ (díodo sentido contrário)}$$

$$18) P_Z = 0,5W = V_Z I_Z$$

$$V_Z \times I_Z = 0,5 \Leftrightarrow 2,4V \times I_Z = 0,5W$$

\Downarrow

$$\Leftrightarrow I_Z = 208 \text{ mA}$$

$$5 - 0,6 - 2,4 = R \times 208 \text{ mA}$$

$$\Leftrightarrow \frac{2}{208 \times 10^{-3}} = R \quad \Leftrightarrow R = 9,6 \Omega \quad R : c$$

$$19) V_{SP} = V_{RMS} \times \sqrt{2} \Leftrightarrow V_{SP} = 16\sqrt{2} \Leftrightarrow V_{SP} = 22,6V$$

$$V_{LMAX} = V_{SP} - 2 \times V_{pp} = 21V \quad V_{ripple} = 2V$$

\Downarrow

$$22,6V \qquad \qquad 0,8V$$

$$V_{Lmed} = V_{LMAX} - \left(\frac{V_{ripple}}{2} \right) = 21 - 1 = 20V$$

$$i_{Lmed} = \frac{V_{Lmed}}{20\Omega} \approx 1A \quad C = \frac{i_{Lmed}}{2\pi \times V_{ripple}} = \frac{1}{100 \times 2} = \frac{1}{200} = 5000 \mu F$$

\Downarrow

$$R_L$$

$$20) V_y = 0,6V \quad V_z = 12V$$

$$f = 50 \text{ Hz} \quad V_{\text{eff}} = 16$$

$$V_{ip} = 16 \times \sqrt{2} = 22,6V$$

$$I_2 = \frac{V_z}{1200} = \frac{12}{1200} = \frac{1}{100} = 0,01 \text{ A} = 10 \text{ mA}$$

$$V_{ip} - 0,6 - V_z = 400 \Omega \times I_1 \Leftrightarrow 22 - 12 = 400 \times I_1$$

$$\Leftrightarrow \frac{10}{400} = I_1 \Leftrightarrow I_1 = 25 \text{ mA} \rightarrow \text{Kirchhoff da malha da esquerda}$$


R: $I_z = I_1 - I_2 = 25 - 10 = \underline{\underline{15 \text{ mA}}}$

$$8) I_1 = 1A \quad V_{AB} = 1V$$

$$I_2 = \frac{1}{2} = 0,5A \quad I_3 = I_2 + I_1 \quad \text{e} I_3 = 1,5A$$

$$V_{CA} = 2 \times \frac{3}{2} = 3V$$

$$V_{CB} = 1 + 3 = 4V$$

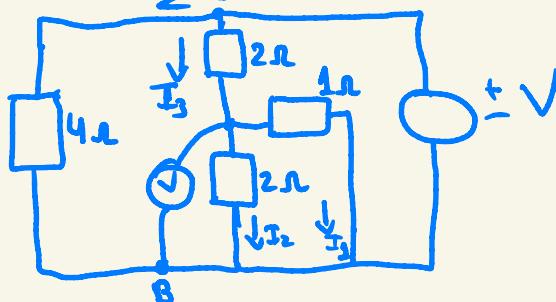

Teste 2018

① D

② $i_2 = i_{2A} + i_{2B}$ ($\rightarrow i_2 = 1 - 0,5 = 0,5A$)

$$\frac{R_L}{R_L + R_s} \times I$$

$$i_{2A} \rightarrow \frac{5}{5+15} \times 4 = \frac{20}{20} = 1A$$

$$i_{2B} \rightarrow \frac{5}{5+15} \times (-2) = \frac{-10}{20} = -0,5A$$

③

$$\textcircled{11} \quad Z = \sqrt{(R)^2 + \left(\frac{j}{\omega C}\right)^2} = 2000 \Omega$$

$$4 \times 10^6 - 1 \times 10^6 = \left(\frac{1}{\omega C}\right)^2$$

$$\Leftrightarrow \left(\frac{1}{\omega C}\right)^2 = 3 \times 10^6 \Leftrightarrow \frac{1}{\omega C} = 1732 \Rightarrow \omega C = \frac{5,72}{10^4}$$

$$\omega = \frac{5,72 \times 10^{-4}}{10^{-6}} \Leftrightarrow \omega = 577$$

$$f = \frac{\omega}{2\pi} \Leftrightarrow f = 91,8 \text{ Hz}$$

$$\textcircled{12} \quad I_1 = \frac{2,71}{1800} = 1,8 \text{ mA}$$

$$I_2 = \frac{13,55}{1800} = 2,88 \text{ mA}$$

$$\begin{aligned} V_{AB} &= (3300 + 2700) I_1 + 2,71 \\ &= 10,84 + 2,71 = 13,55 \end{aligned}$$

$$I_3 = I_1 + I_2 \Leftrightarrow I_3 = 1,8 + 2,88 \simeq 4,7 \text{ mA}$$

$$\textcircled{6} \quad V = \frac{1}{C} \int_0^{0,1} i dt + y_0^0$$


$$\textcircled{7} \quad V = \frac{1}{C} i T$$

$$\textcircled{7} \quad V = \frac{1}{0,0005} \times 10 \times 10^{-3} \times 0,1$$

$$\textcircled{7} \quad V = 2000 \times 10^{-4}$$

$$\textcircled{7} \quad V = 2 \text{ V}$$

Teste tipo 2023

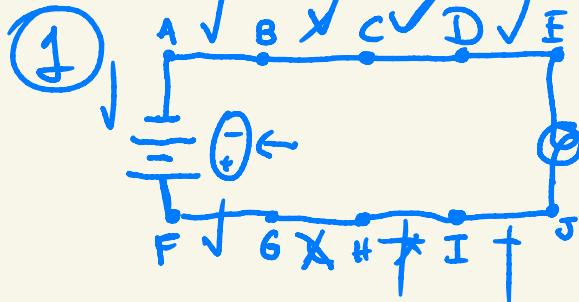


Tensão entre B e G: 12V
 " " C e I: 0V
 " " E e G: 12V
 " " E e H: 0V

C


2 período de tempo infinito C

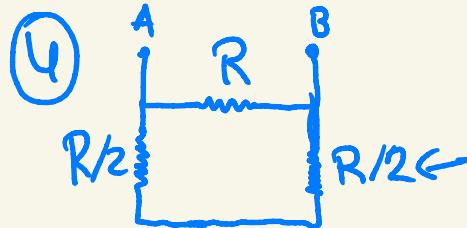3 $i_1 + i_2 + i_3 = 0 \quad (1) \quad 2 - 3 + x = 0$
 $(2) \quad x = 1A \quad C$




$$\frac{R}{2} + \frac{R}{2} = R$$
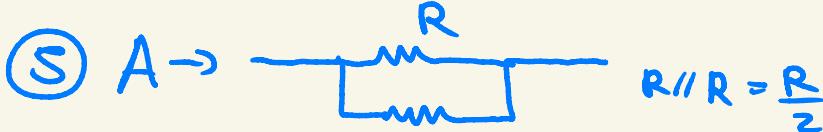
$$R // R = \frac{R^2}{2R} = \frac{R}{2} \quad C$$



Ordem: DBCA

A

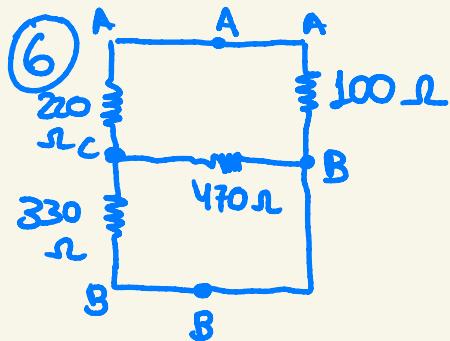

$$R = \frac{470 \times 330}{470 + 330} + 220$$

$$\approx R = 413,875$$

$$R_{eq} = \frac{413,875 \times 100}{413,875 + 100} \text{ w/ } R_{eq} = 80,5 \Omega$$

(A)

7 $V_1 = \frac{790 // 8600}{790 // 8600 + 1000} \times 32$


$$\approx V_1 = \frac{\frac{790 \times 8600}{790 + 8600}}{\frac{790 \times 8600}{790 + 8600} + 1000} \times 32$$

$$\approx V_1 = 13,43V$$

$$I_2 = -\frac{V_2}{8,6k} \text{ w/ } I_2 = -\frac{13,43}{8600} \text{ w/ } I_2 = -1,56 \text{ mA}$$

(A)

Sentido
Contrário

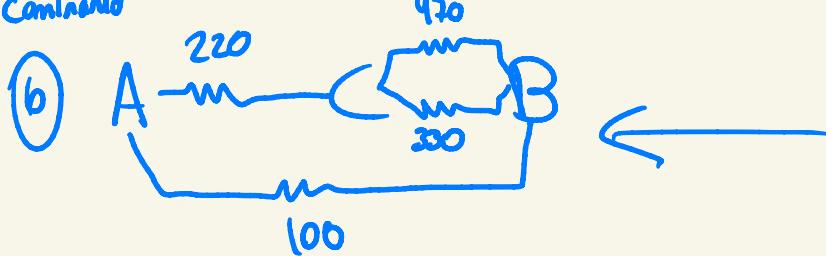

$$\textcircled{8} \quad d \quad |V_s| = \sqrt{|V_a|^2 + |V_c|^2}$$

$$\textcircled{9} \quad V = \frac{I}{G} \Leftrightarrow V = \frac{0,5 + 0,3}{0,01 + 0,04}$$

$$\Leftrightarrow V = \frac{0,8}{0,05} \Leftrightarrow V = 16V$$

$$I = I_{S1} - I_1 \Leftrightarrow I = 0,5 - (16 \times 0,01)$$

$$\Leftrightarrow I = 0,34 A \quad \textcircled{c}$$

$$\textcircled{10}$$

$$V_D = \frac{2k\Omega}{4k\Omega + 1k\Omega + 2k\Omega} \times 10,5$$

$$\Leftrightarrow V_D = 3,19V$$

$$V_{AD} = V_A - V_D \Leftrightarrow V_{AD} = 10,5 - 3,19 \Leftrightarrow V_{AD} = 7,31V$$

\textcircled{A}

$$\textcircled{11} \quad |Z_t| = 4k\Omega \text{ at } 100\text{Hz} \quad R = 2200$$

$$C = \frac{1}{2\pi j \sqrt{|Z_t|^2 - R^2}} \Leftrightarrow C = \frac{1}{2\pi \times 100 \sqrt{4000^2 - 2200^2}} \quad \text{calc} = \frac{1}{200\pi \sqrt{3340}}$$

$$\Leftrightarrow C = 4,8 \mu F \quad \textcircled{A}$$

$$|Z_t| = \sqrt{R^2 + \left(\frac{1}{j\omega C}\right)^2}$$

$$12) V_{eg} = \sqrt{\frac{1}{T} \int_0^{100} v(t)^2 dt}$$

$$\Leftrightarrow V_{eg} = \sqrt{\frac{1}{100\mu} \times \left(\int_0^{50} 8^2 dt + \int_{50}^{100} (-2)^2 dt \right)}$$

$$\Leftrightarrow V_{eg} = \sqrt{\frac{1}{100\mu} \times [64t]_0^{100} + [4t]_0^{50}}$$

$$\Leftrightarrow V_{eg} = \sqrt{\frac{1}{100\mu} \times (0,00064 + 0,00036)}$$

$$\Leftrightarrow V_{eg} = \sqrt{\frac{1}{500 \times 10^{-6}} \times 0,001} \Leftrightarrow V_{eg} = \sqrt{\frac{0,001}{500 \times 10^{-6}}} \Leftrightarrow V_{eg} = \sqrt{0,002}$$

$$\Leftrightarrow V_{eg} = 3,16 \text{ V } A$$

$$13) V_{out} = \frac{Z_{C_2}}{Z_{C_2} + Z_{C_1}} V_{im}$$

$$\Leftrightarrow V_{out} = \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_2} + \frac{1}{j\omega C_1}} \times V_{im}$$

$$\Leftrightarrow V_{out} = \frac{C_1}{C_1 + C_2} \times V_{im} \Leftrightarrow V_{out} = \frac{0,1 \times 10^{-6}}{0,1 \times 10^{-6} + 0,47 \times 10^{-6}} \times 10$$

$$\Leftrightarrow V_{out} = \frac{0,1}{0,1 + 0,47} \times 10 \Leftrightarrow V_{out} = 1,75 \text{ V}$$

$$\textcircled{14} \quad |G| = 20 \log \left(\frac{R_1}{R_2} \right) \Leftrightarrow |G| = 20 \log \left(\frac{150 \times 10^3}{68 \times 10^3} \right)$$

$$R_1 = 150 \text{ k}\Omega$$

$$R_2 = 68 \text{ k}\Omega$$

$$\Leftrightarrow |G| = 6,87 \text{ dB}$$

$$\textcircled{15} \quad G = G_1 \times G_2 \xrightarrow{\text{Inversora}}$$

$$\Leftrightarrow G = \left(-\frac{12}{1,8} \right) \times \left(1 + \frac{6,8}{4,7} \right) \xleftarrow{\text{Ganho não inversora}}$$

$$\Leftrightarrow G = -16,31 \text{ } \textcircled{a}$$

\textcircled{16} Vai variar entre -0,7V e 8V

$$-8 + V_R^{20} + V_o = 0 \Leftrightarrow V_o = 8V \text{ } \textcircled{a}$$

$$\textcircled{17} \quad V_s = 30V$$

$$-30 + V_R + 0,7 + 10 = 0$$

$$\Leftrightarrow V_R = 30 - 10,7 \Leftrightarrow V_R = 19,3V$$

$$I = \frac{19,3}{100} \Leftrightarrow I = 0,193 \Leftrightarrow I = 193 \text{ mA}$$

$$\textcircled{18} \quad I_z = I_1 - I_2$$

$$\Leftrightarrow I_z = \frac{15 - 5,1}{500} - \frac{5,1}{1000} \Leftrightarrow I_z = 14,7 \text{ mA}$$

I_2 sentido oposto ao diodo

$$\textcircled{19} \quad I_z = 0 \quad I_1 = \frac{15}{4k + 1k} \Leftrightarrow I_1 = 3 \text{ mA}$$

\textcircled{5}

\textcircled{20} 2